


EE 577a Lab4

Spring 2017


Huayu Fu  
4745159848  
3/24/2017

## Part A: Pipelined 5 bit 2's complement Multiplier Design
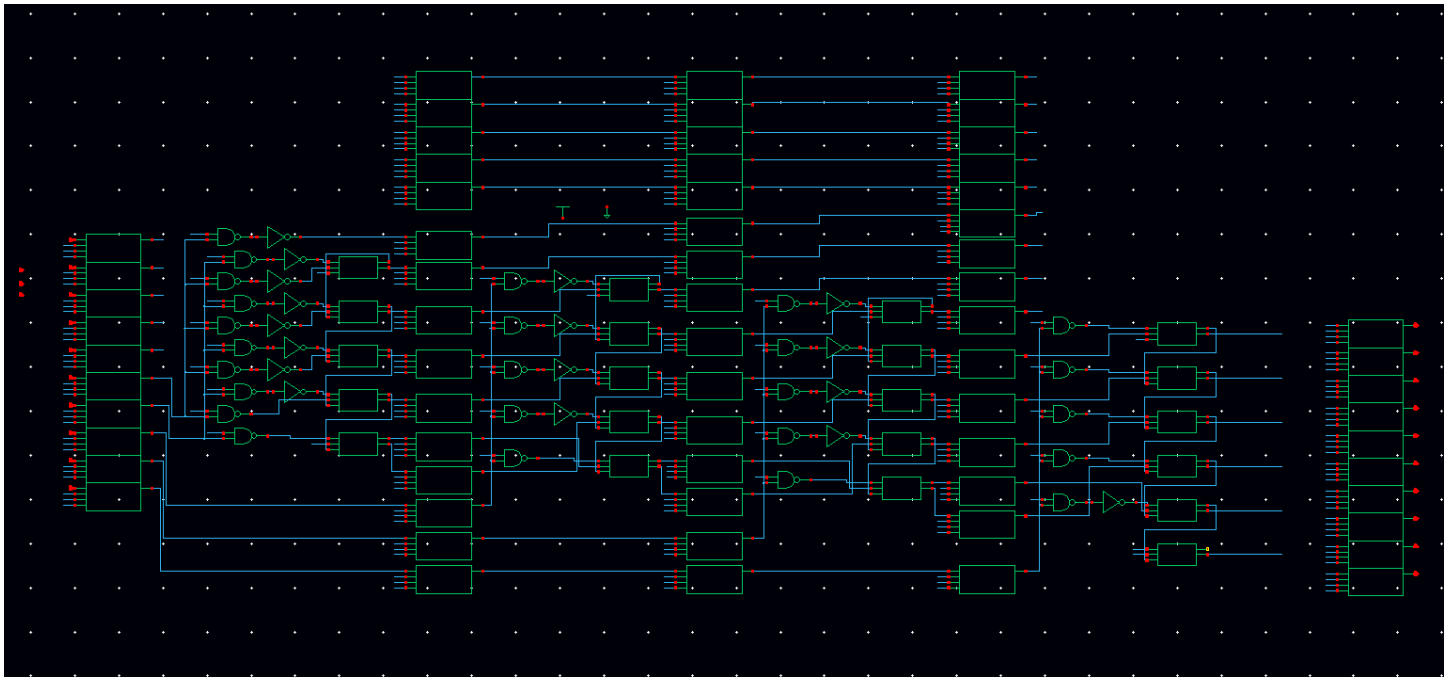
### a) Schematic of the 5-bit Pipelined 2's Complement Multiplier.


 
### b) Functional test waveforms and results of the 5-bit Pipelined 2's Complement Multiplier for 10 random test cases and 5 directed test cases.



### c) Write a front-end perl/python script to generate random test-cases and directed test cases and golden\_results.txt that contains golden results for the 15 test cases. Also write a backend script to write the obtained results from cadence (.csv file) to actual\_results.txt and compare golden results to actual results.

```

import random
def LFSR(start_state):
    start_state=start_state%32
    lfsr=start_state
    l=[]
    while True:
        bit=((lfsr>>0)^ (lfsr>>2))&1
        lfsr=((lfsr)>>1) | ((bit)<<4)
        l.append(lfsr)
        if lfsr==start_state:
            break
    return l
def rawGen(number1,number2,out):
    if (number1>=16):
        number1=(number1%32)-32
    if (number2>=16):
        number2=(number2%32)-32
    number=number1*number2
    out.write(str(number)+"\n")

def main():
    out=open('golden_result.txt','w')
    out1=open('testcase.vec','w')
    out2=open('BinaryInput.txt','w')
    out1.write("radix\t1\t4\t1\t4\t1\t4\t1\t1\n")
    out1.write("io\t1\t1\t1\t1\t1\t1\t1\n")
    out1.write("vname\t4\t4\t4\t4\t4\t4\t4\t4\n")
    out1.write("slope\t0.01\n")
    out1.write("vih\t1.8\n")
    out1.write("tunit\t1\n")
    l=LFSR(47)
    period=1.8
    for i in range(10):
        ola=str((i*period)+'\t')
        olb=str((i+0.5)*period)+'\t'
        number1=l[random.randint(0, len(l)-1)]
        ola+=str(number1/16)+'\t'
        ola+=hex(number1%16)[2]+' \t'
        olb+=str(number1/16)+'\t'
        olb+=hex(number1%16)[2]+' \t'
        for x in range(4,-1,-1):
            bit=(number1%(pow(2,x+1)))/pow(2,x)
            if (x==0):
                out2.write(str(bit)+'\t')
            else:
                out2.write(str(bit))
        number2=l[random.randint(0, len(l)-1)]
        ola+=str(number2/16)+'\t'
        ola+=hex(number2%16)[2]+' \t'
        olb+=str(number2/16)+'\t'
        olb+=hex(number2%16)[2]+' \t'
        ola+="0\t1\n"
        olb+="1\t0\n"
        out1.write(ola)
        out1.write(olb)
        for x in range(4,-1,-1):
            bit=(number2%(pow(2,x+1)))/pow(2,x)
            if (x==0):
                out2.write(str(bit)+'\n')
            else:
                out2.write(str(bit))
        rawGen(number1,number2,out)
    a=[1, 15, 16, 15, 0, 0, 0, 0, 0, 0, 0]
    b=[31, 15, 16, 16, 0, 0, 0, 0, 0, 0, 0]
    for i in range(len(a)):
        ola=str((i+10)*period)+'\t'
        olb=str((i+10.5)*period)+'\t'
        number1=a[i]
        ola+=str(number1/16)+'\t'
        ola+=hex(number1%16)[2]+' \t'
        olb+=str(number1/16)+'\t'
        olb+=hex(number1%16)[2]+' \t'
        for x in range(4,-1,-1):
            bit=(number1%(pow(2,x+1)))/pow(2,x)
            if (x==0):
                out2.write(str(bit)+'\t')
            else:
                out2.write(str(bit))
        number2=b[i]
        ola+=str(number2/16)+'\t'
        ola+=hex(number2%16)[2]+' \t'
        olb+=str(number2/16)+'\t'
        olb+=hex(number2%16)[2]+' \t'
        ola+="0\t1\n"
        out1.write(olb)
        for x in range(4,-1,-1):
            bit=(number2%(pow(2,x+1)))/pow(2,x)
            if (x==0):
                out2.write(str(bit)+'\n')
            else:
                out2.write(str(bit))
        rawGen(number1,number2,out)
    out.close()
    out1.close()
    out2.close()
if __name__ == "__main__": main()

```



BinaryInput.txt - Notepad				golden_result.txt - Notepad				
File	Edit	Format	View	File	Edit	Format	View	Hel
10100		10010		168				
11001		11001		49				
00111		11000		-56				
01110		00011		42				
10011		00101		-65				
00111		00011		21				
11001		01001		-63				
01000		01001		72				
00001		10101		-11				
00010		11001		-14				
00001		11111		-1				
01111		01111		225				
10000		10000		256				
01111		10000		-240				
00000		00000		0				
00000		00000		0				
00000		00000		0				
00000		00000		0				
00000		00000		0				
00000		00000		0				
00000		00000		0				
00000		00000		0				


d) Report the minimal clock period that you can achieve.

2ns


## Part B. Pipelined 5-bit 2's Complement Multiplier Optimization

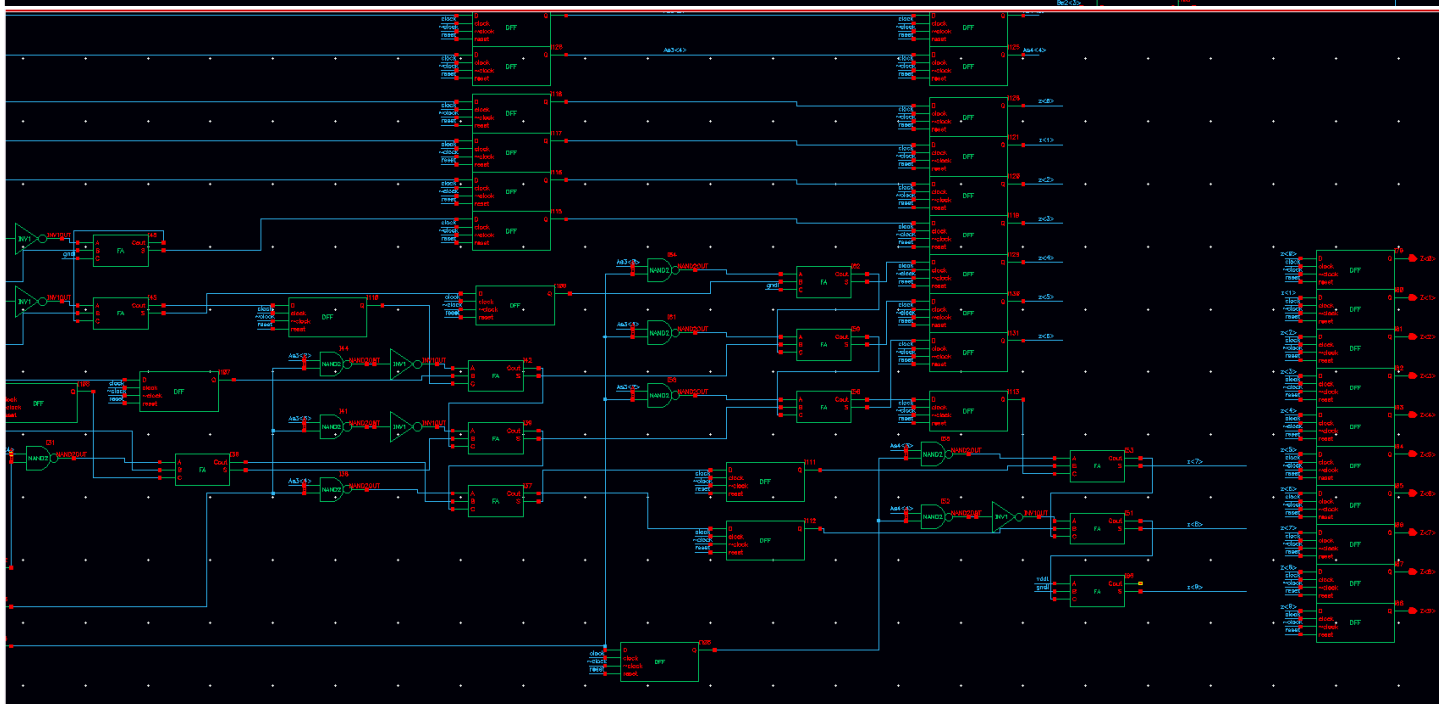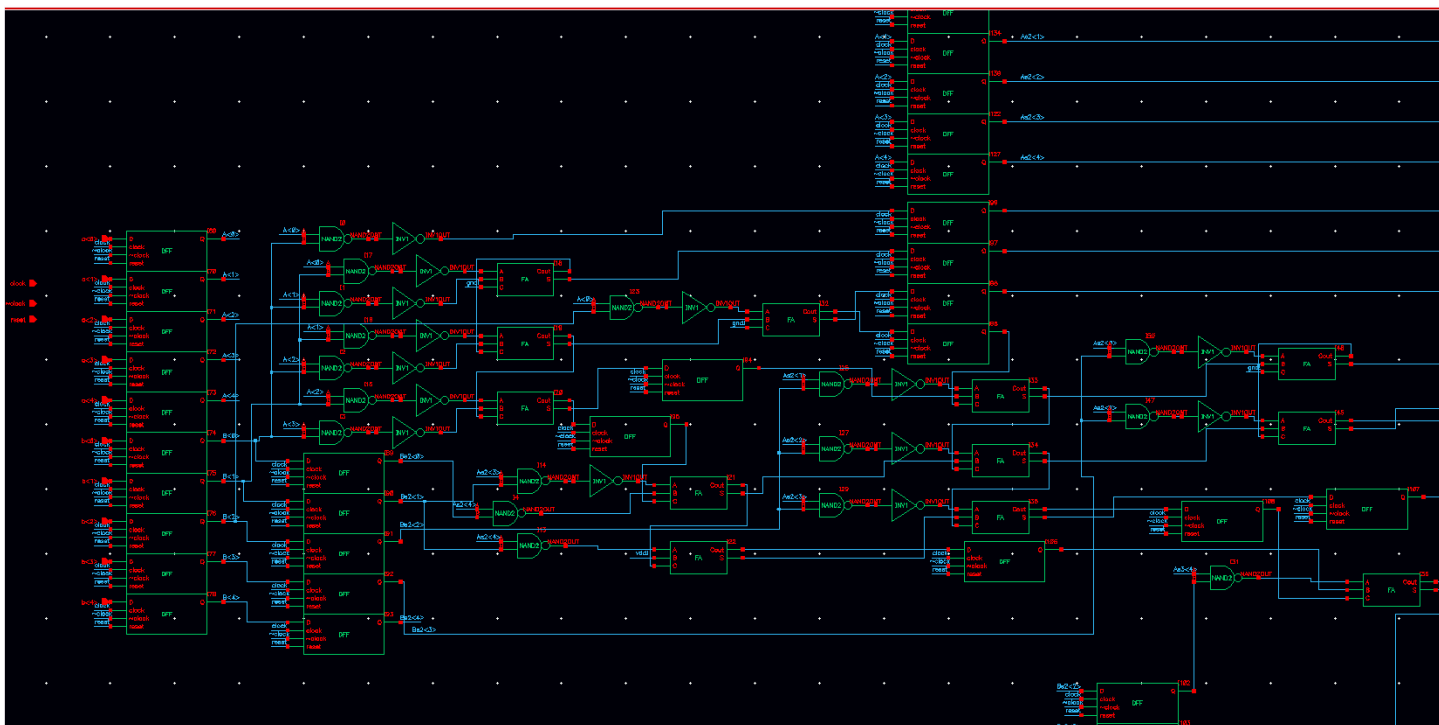e) Schematic and layout of the optimized 5-bit Pipelined 2's Complement Multiplier.



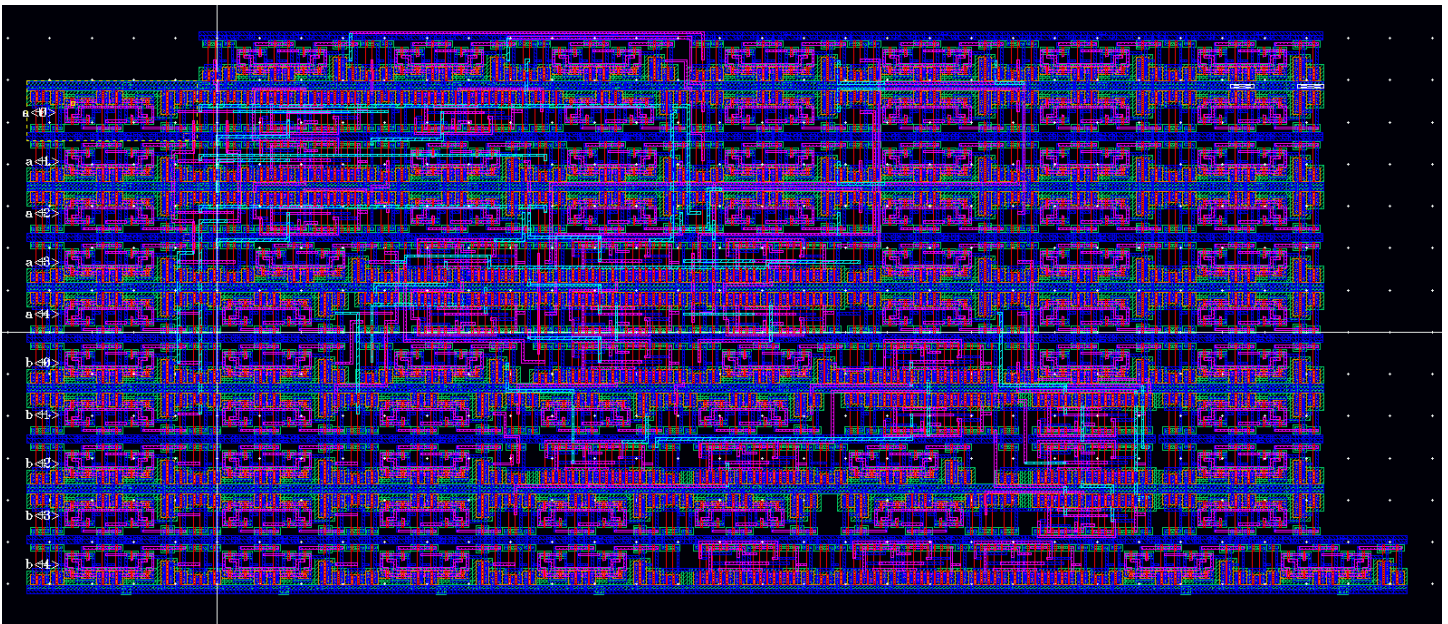

 - f) Functional testwaveforms and results of the 5-bit Pipelined 2's Complement Multiplier for 10 random test cases and 5 directed test cases. The 15 test cases should be the same as what you have used in Part A.



- g) Report the minimal clock period that you can achieve after optimization.

1.4ns

- h) Compare the minimal clock period you achieved in part A and B. Explain the reason why the clock period can be reduced after optimization.

For part A 1.8ns for Part B 1.4ns, 22% improvement, since the critical path is optimized. Each stage a signal goes to at most 3 full adder.

- i) Compare the number of Flip-Flops in part A and B and explain the difference.

PA=142-89+1=53 PB=141-89+1=52 part B saves 1 flip flops