
 




EE577
LAB1 Part2
Report


Huayu Fu
2/3/2017

1- bit Full Adder

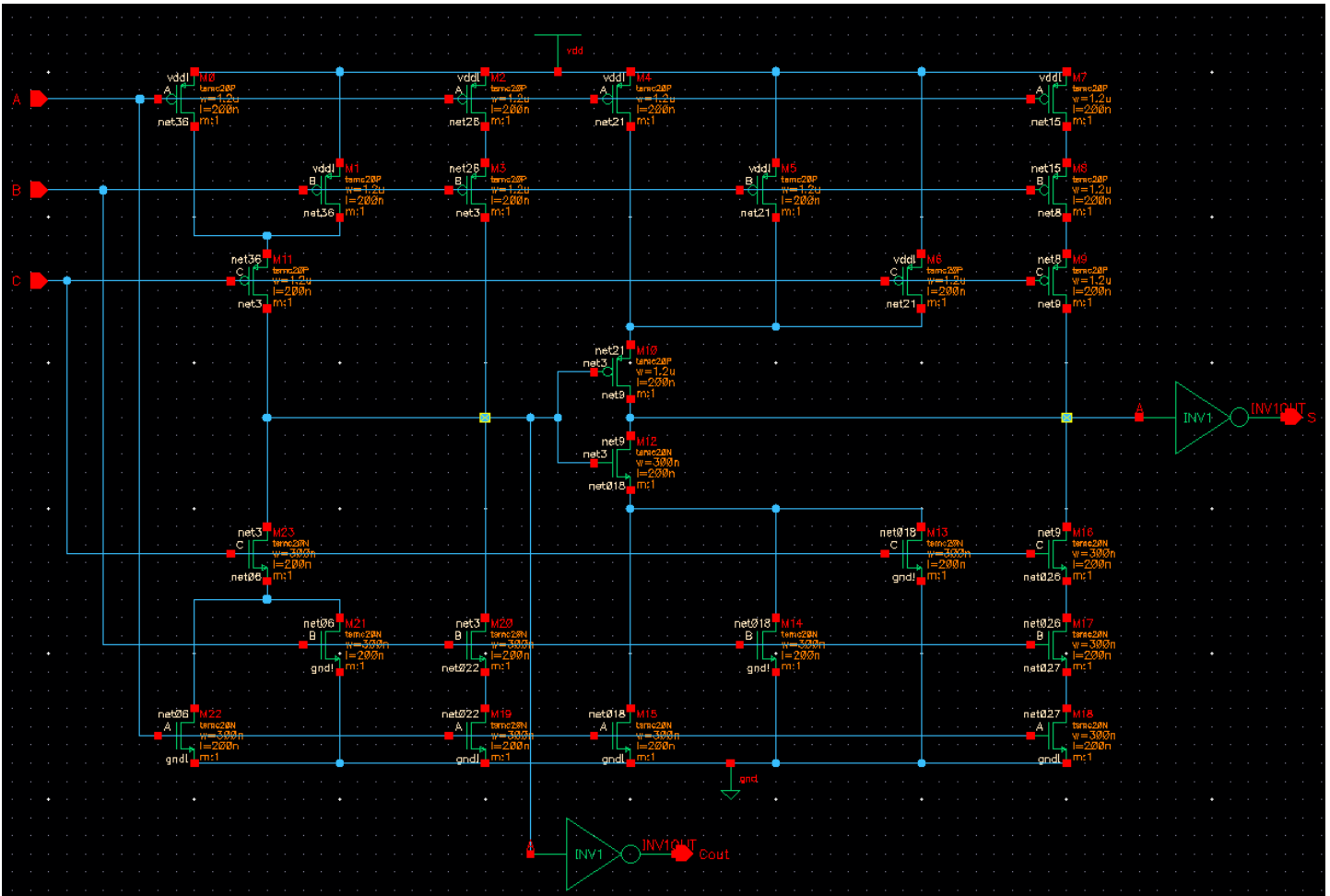
1. Schematic, symbol and layout.
 - a. Standard full adder



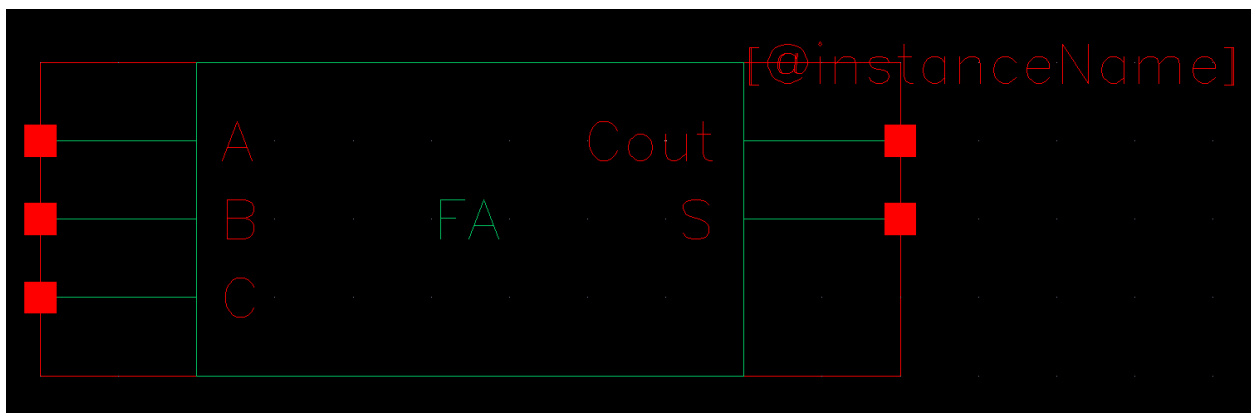 


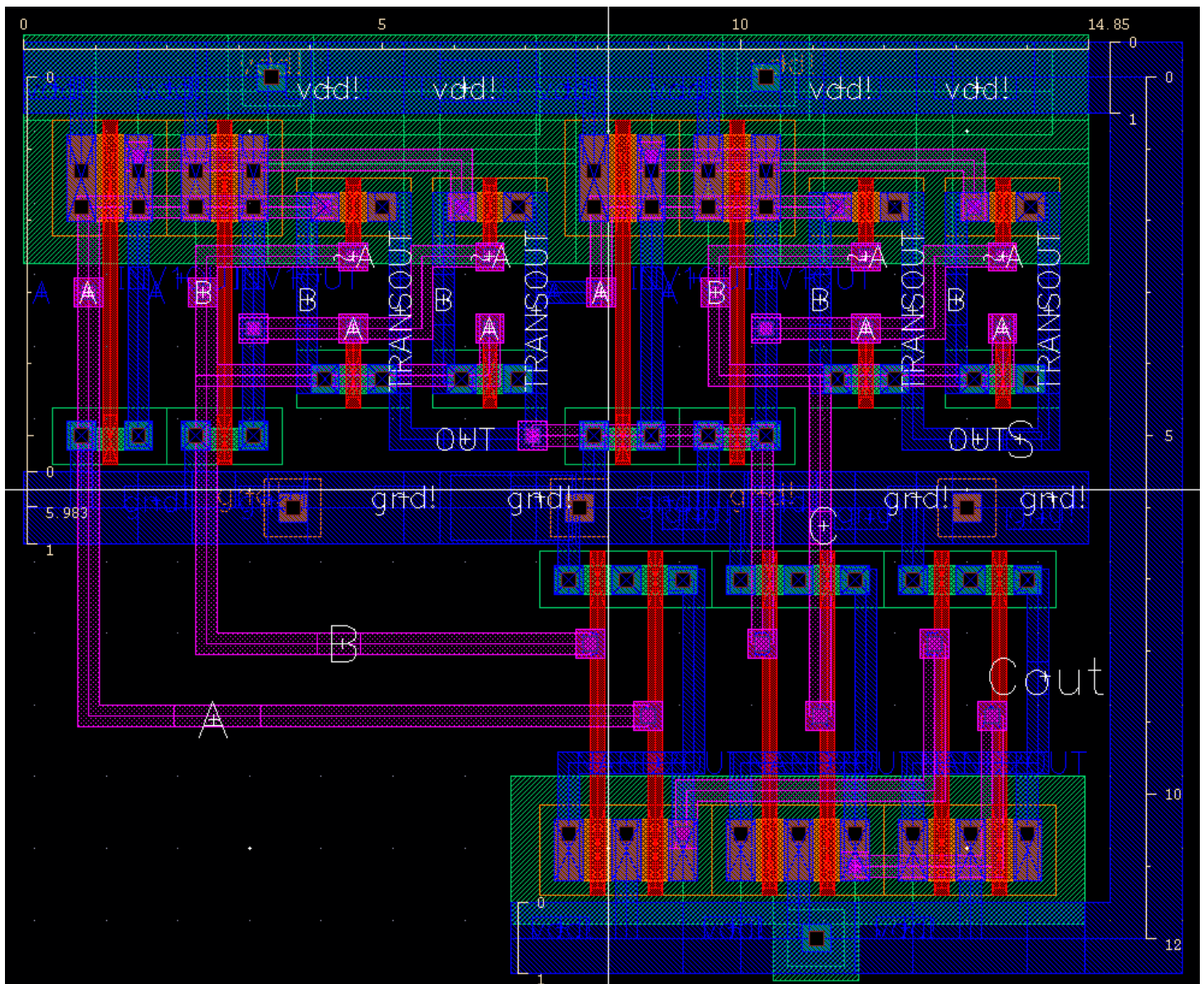

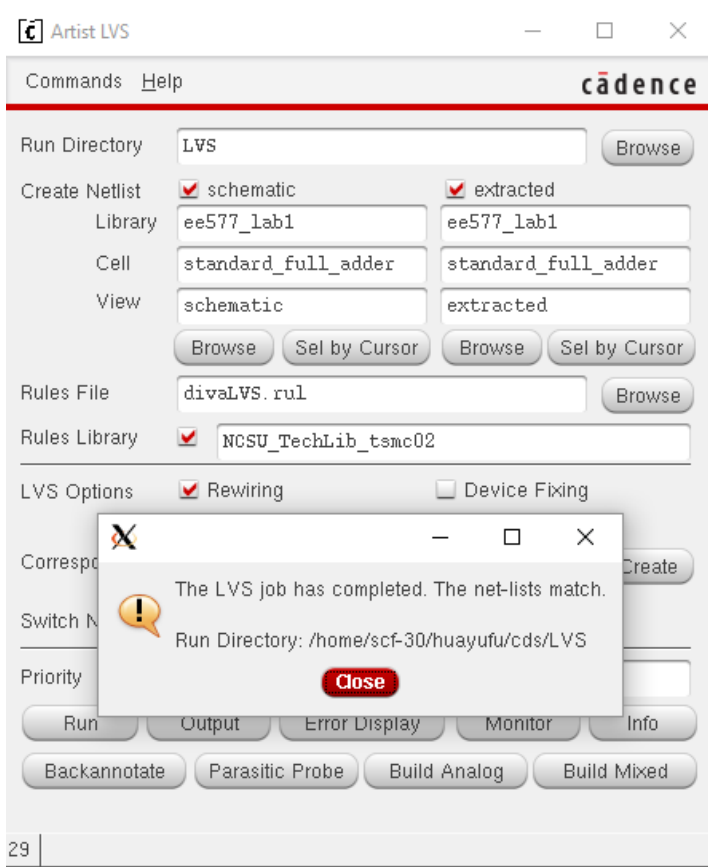
2. Metal width=1 um, height of cell=6 um
 - a. Standard full adder
Total area=15.2*6=91.2 um²
 - b. Gate level full adder
Total area=14.85*12=178.2 um²
3. LVS
 - a. Standard full adder



b. Gate level full adder

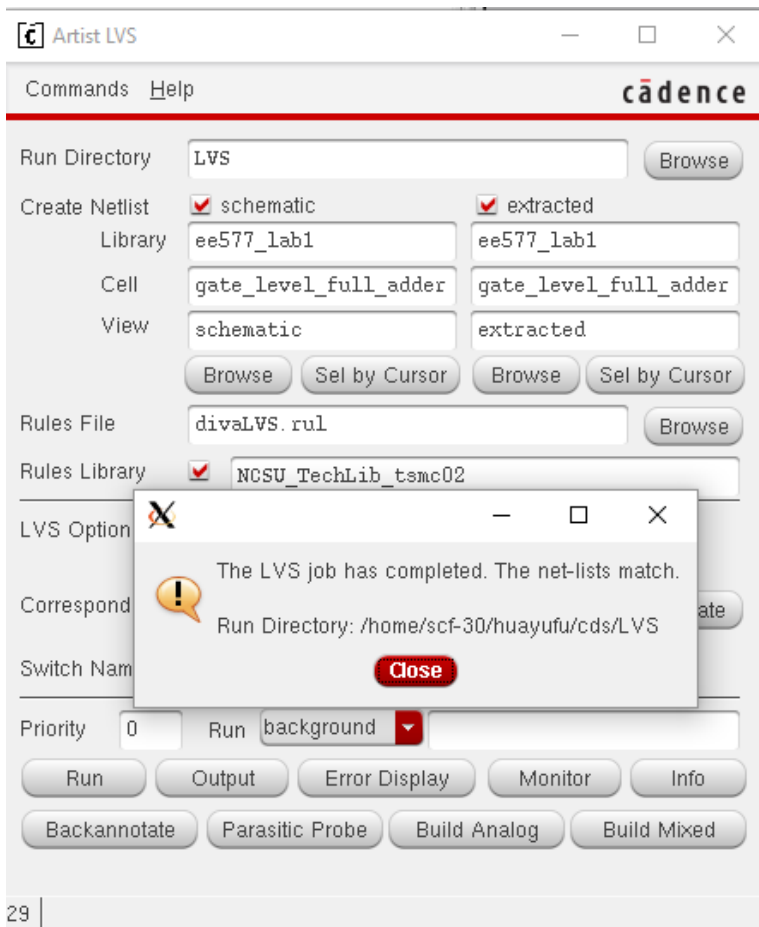

4. Function test
a. Standard full adder

 

b. Gate level full adder





5. Comparison results and explanation.

Standard Full Adder					Gate level Full adder				
C	S	S delay	Cout	Cout delay	C	S	S delay	Cout	Cout delay
1.0025	1.1381	0.1356			1.0025	1.0651	0.0626		
3.005	3.2267	0.2217	3.1534	0.1484	3.005	3.0293	0.0243	3.1004	0.0954
4.0017	4.272	0.2703	4.1105	0.1088	4.0017	4.0472	0.0455	4.093	0.0913
5.0033	5.2404	0.2371	5.1751	0.1718	5.0033	5.0295	0.0262	5.1004	0.0971



Conclusion, the gate level design has smaller delay, but the output signal is not smooth during the input changes. The reason for gate level design have smaller delay may because it has smaller capacitance to charge. Each gate is separated.

8-bit Carry-Skip adder



6. Schematic and layout

 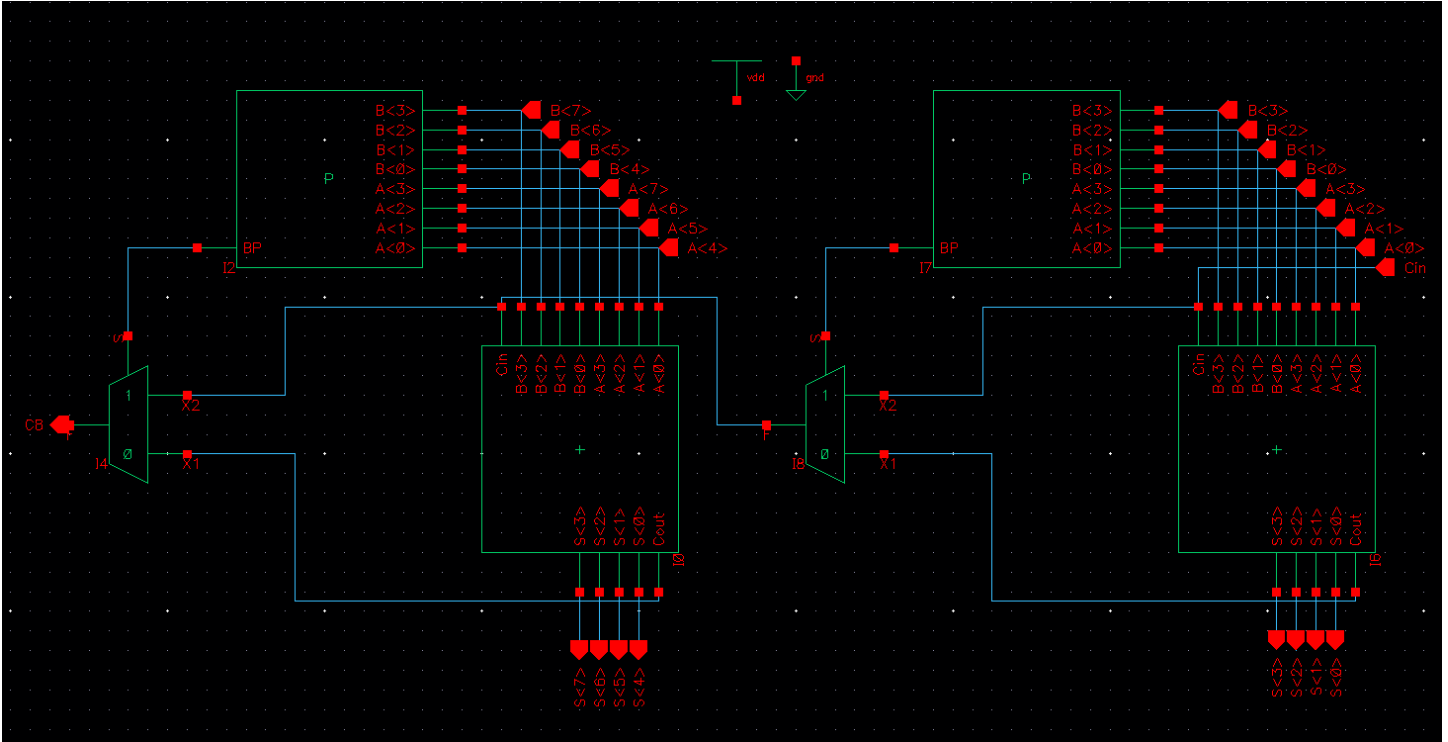



P module

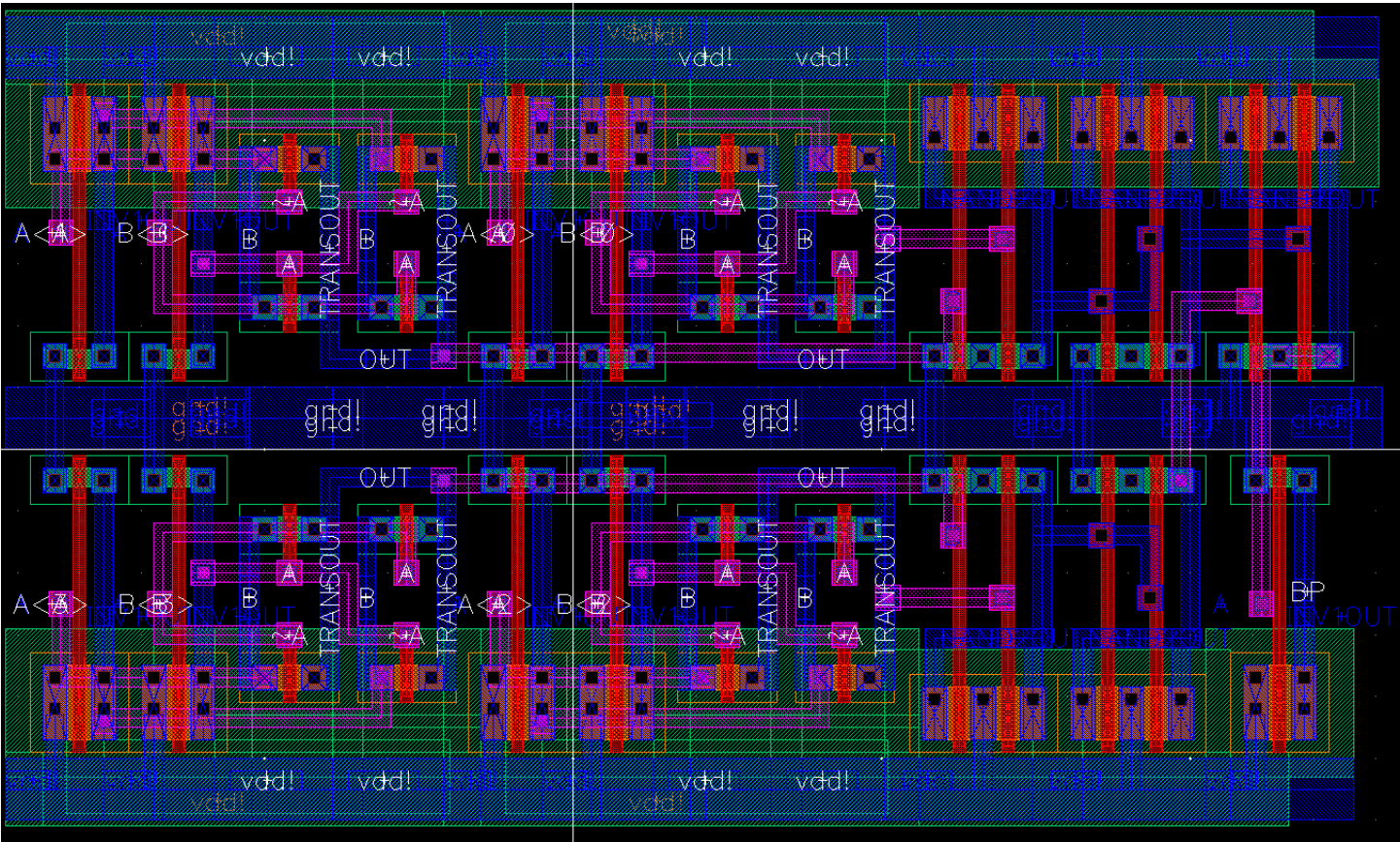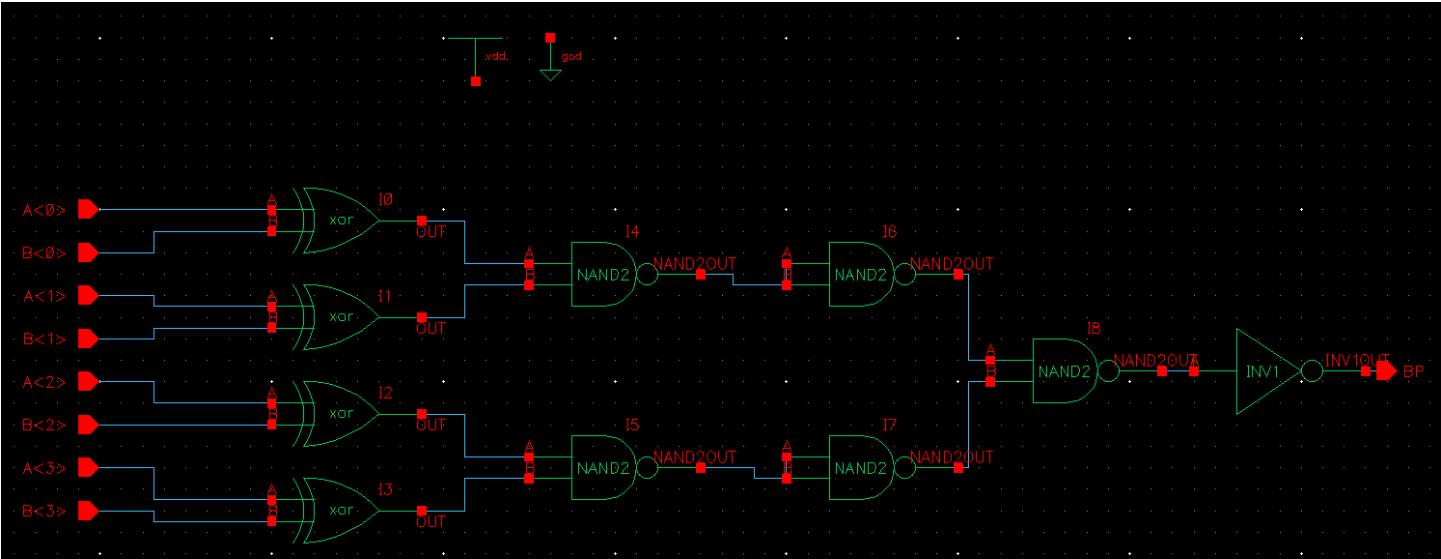

Mux

 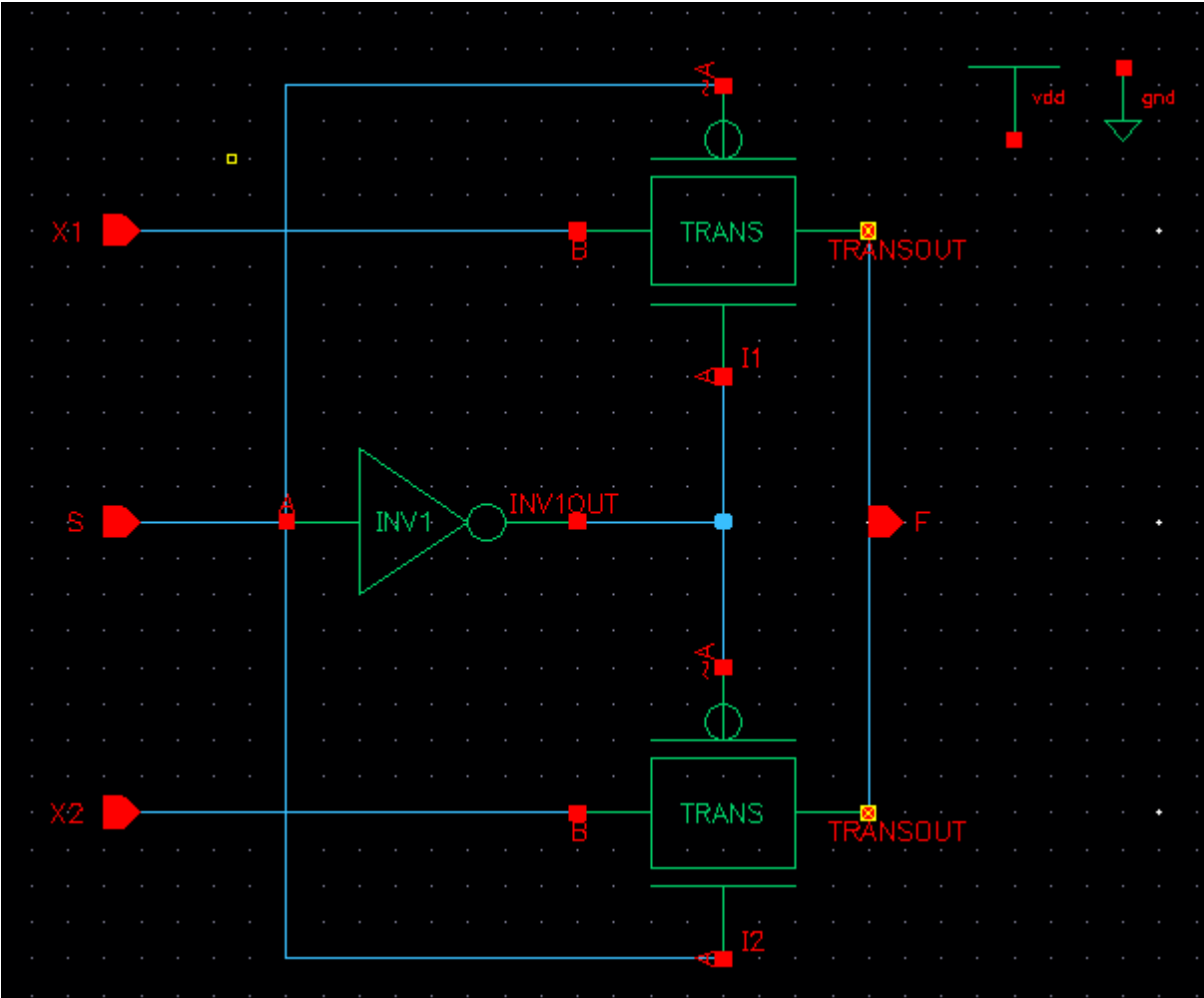


4-bit adder

 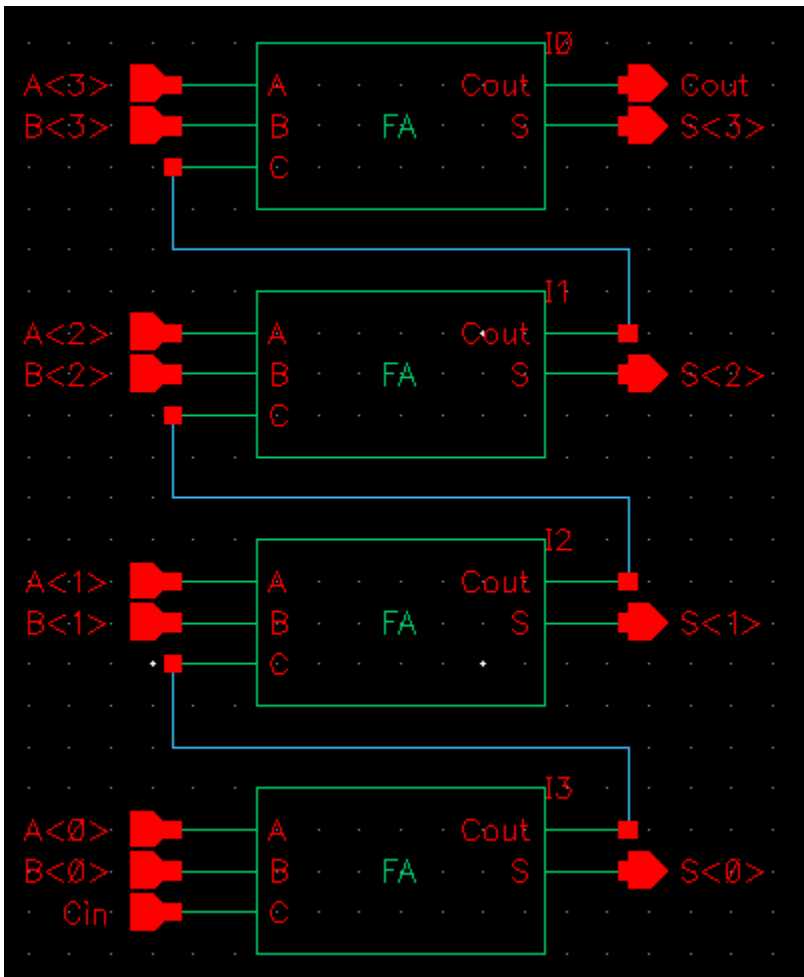

7. Total area=58.4*24=1401.6 μm^2

8. LVS

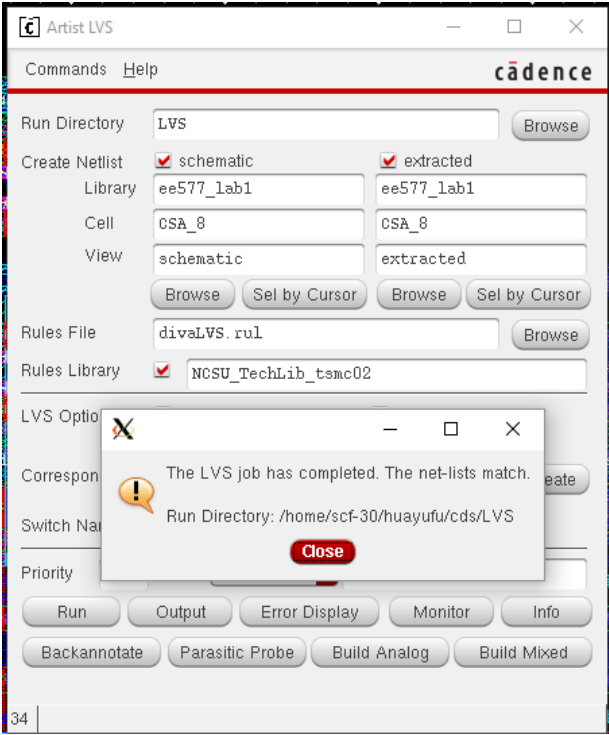


9. Functional test waveforms and results on the layout of 8-bit Carry-skip adder for any six random inputs.

```
radix 4 4 4 4
io i i i i
vname A<[7:4]> A<[3:0]> B<[7:4]> B<[3:0]>
slope 0.01
vih 1.8
tunit ns
0 0 F 0 F
4 F F 0 1
8 0 A 0 B
12 0 C 0 1
16 0 1 0 1
20 1 2 2 1
```



A	B	expected S	actual S
1111	1111	11110	11110
11111111	1	0	0
1010	1011	10101	10101
1100	1	1101	1101
1	1	10	10
10010	100001	110011	110011



Transient Response

 


2's Complement Multiplier

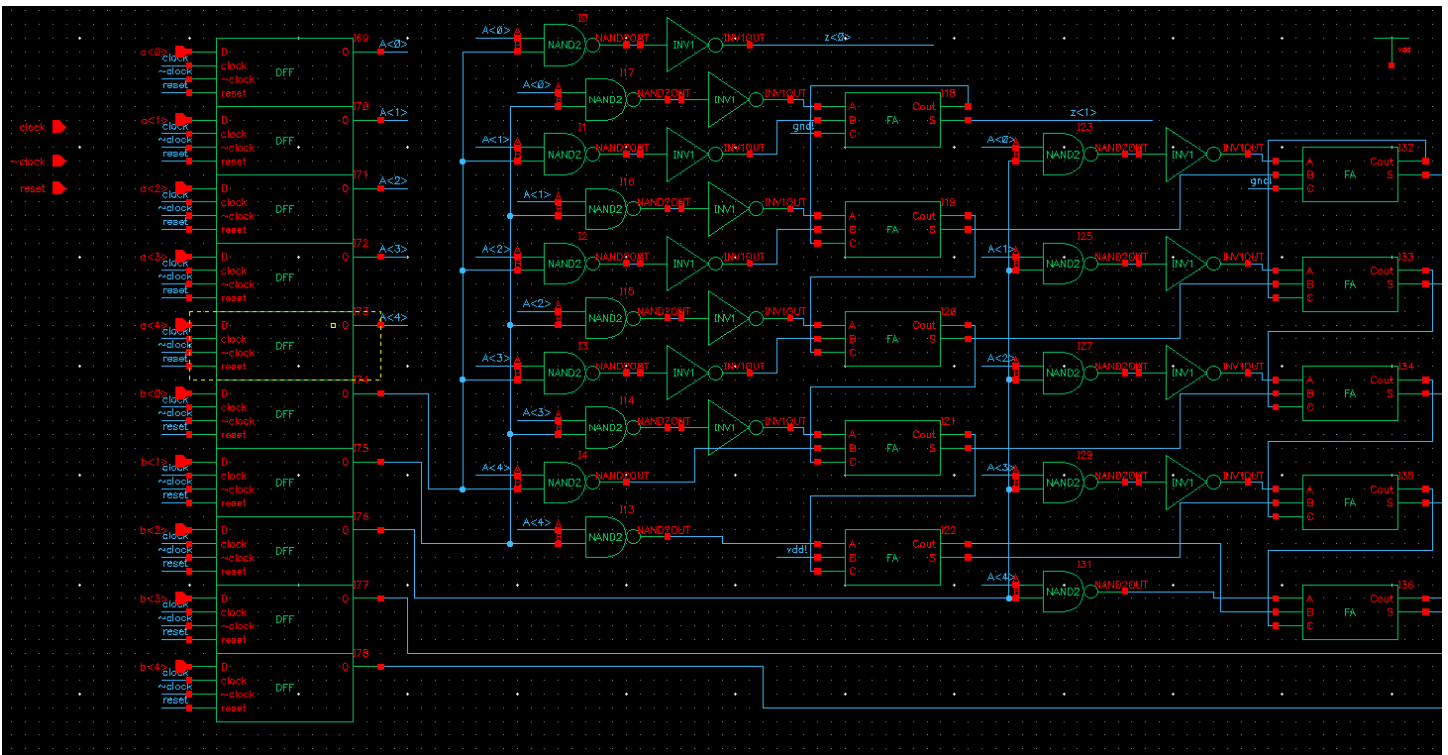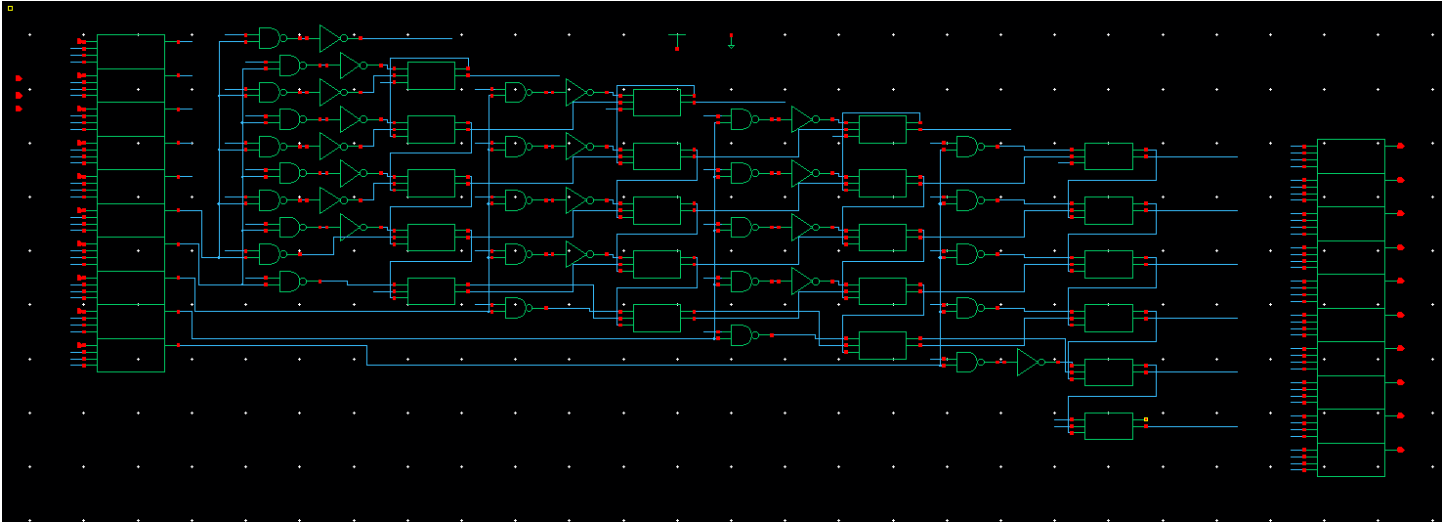10. Schematic and layout for 2's Complement Multiplier.



 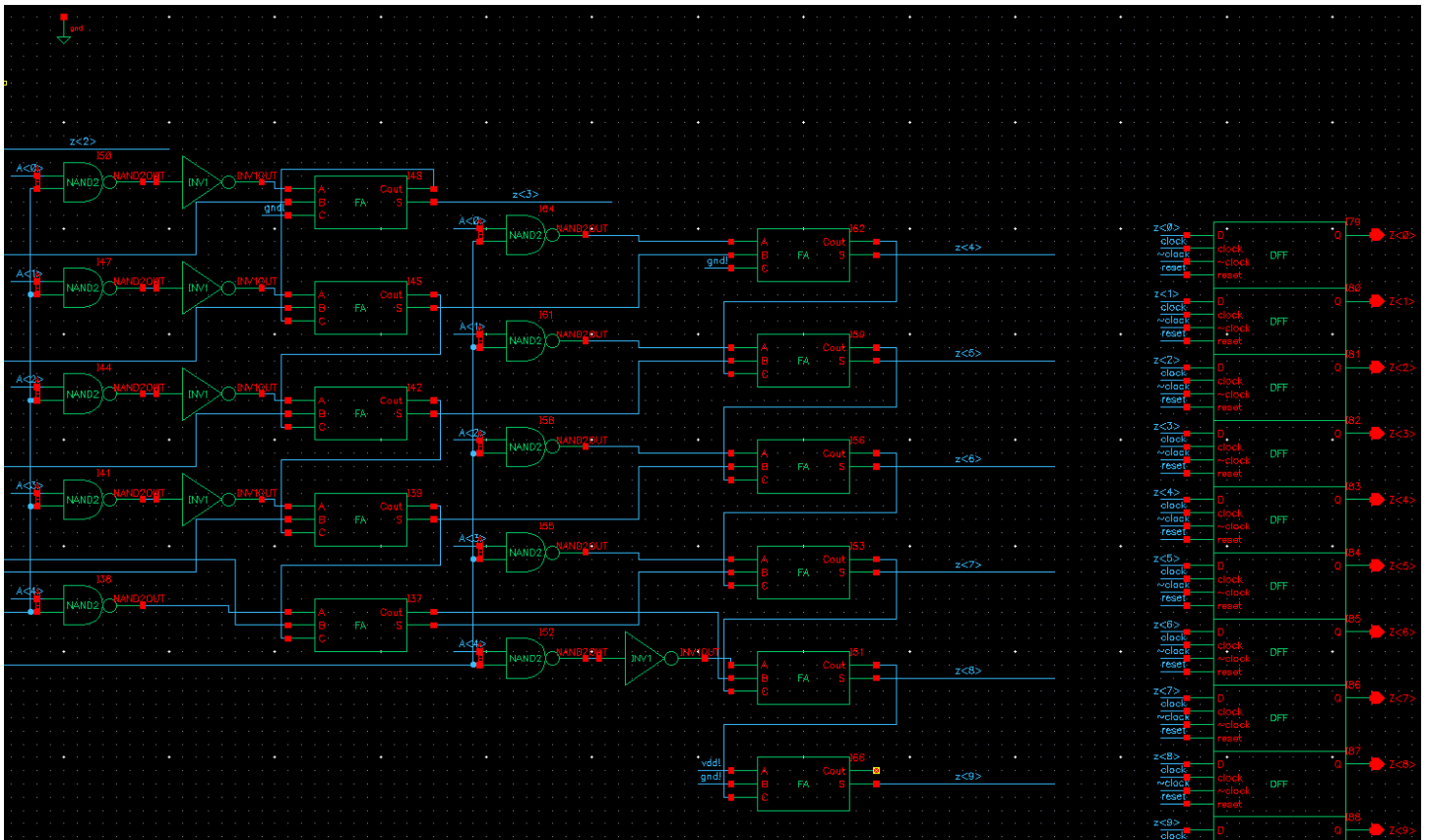

Total area=133*42=5586 um²

 

Artist LVS

Commands Help

cadence

Run Directory: LVS [Browse]

Create Netlist: ☒ schematic ☒ extracted

Library: ee577_lab1 ee577_lab1

Cell: Multiplier Multiplier

View: schematic extracted

[Browse] [Sel by Cursor] [Browse] [Sel by Cursor]

Rules File: divaLVS.rul [Browse]

Rules Library: ☒ NCSU_TechLib_tsmc02

LVS Option

Correspond

Switch Nam

Priority

Run Output Error Display Monitor Info

Backannotate Parasitic Probe Build Analog Build Mixed

The LVS job has completed. The net-lists match.


Run Directory: /home/scf-30/huayufu/cds/LVS

Close

42

Functional Test using Perl or Python

 12. Functional test waveforms and results on the layout of 2's Complement Multiplier for the 5 test



op1	op2	result	op1	op2	restut
10	-10	-100	0b01010	0b10110	1110011100
10	11	110	0b01010	0b01011	0,001,101,110
1	-8	-8	0b00001	0b11000	1111111000
-11	15	-165	0b10101	0b01111	1101011011
-7	-7	49	0b11001	0b11001	0,000,110,001